

A Planar-Triode Phono Preamp

An unlikely looking tube is the star performer in this smooth-sounding preamp **By Eric Barbour**

After having worked in tube audio as a “professional,” i.e., getting paid by an actual employer that sold tubes, I’ve gained some useful insights into tube design. Some of this knowledge actually applies to the common circuit designs that see frequent use. More to the point, I learned the personal motivations of many designers of said equipment.

You might be surprised to learn how much of the use of a given tube is based upon pricing, not on technical merit. All of the largest OEMs of high-end audio equipment seem unwilling to pony up a large sum for development of a tube to meet their strict requirements. Instead, they prefer to constantly call tube distributors and factories and try to wheedle them into selling for a lower price. If a fraction of this effort was used to redesign their products using available tubes, all of their problems would go away.

The hobbyist has a tremendous advantage here, by simply keeping an open mind. Instead of chasing down a price that is one penny lower for Russian 6922s, he can use tubes that are readily available, and are vastly better performers than the lowly 6922. Ironically, some outstanding Russian tubes are never used in audio equipment, yet happen to be excellent for audio use.

HISTORY

The 6922/6DJ8 has been used for years in audio, because of its low cost, detailed sound qualities, and (alleged) low noise figure. I find this ironic, because it is a frame-grid triode, and there are far more sophisticated and

quieter frame-grid triodes. The first frame-grid triode, in fact, was a very odd-looking tube in a metal canister—the Western Electric 416A of 1948. In spite of its very high Gm (equating to very low noise), audiophiles have no interest in it or its metal-cased cousins. Instead, they seek frame-grid types in conventional glass envelopes.

While a WE 437A can sell for as much as \$600 on eBay, a 416D (a far superior device) usually sells for less than

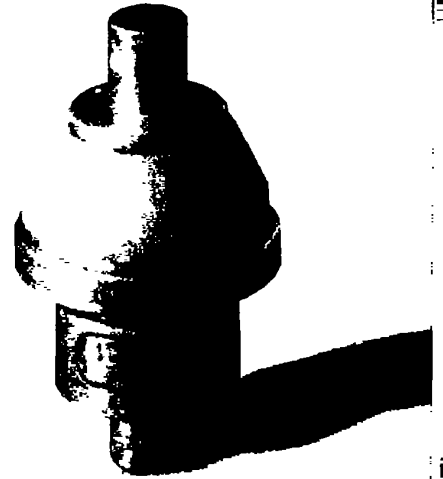


PHOTO 1: 6S17K-V tube.

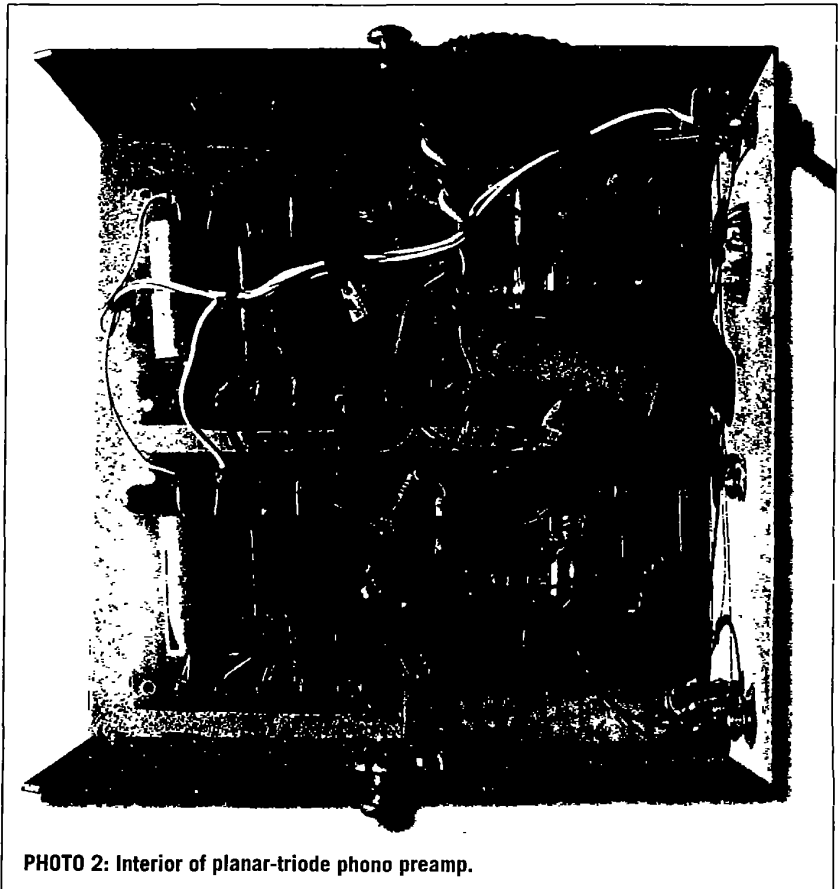


PHOTO 2: Interior of planar-triode phono preamp.

W

All consi
fantastic
for the m

New at
AC No

IN STOCK
Nordost

LINE

\$100. Reasons? Apparently, the difficulty of finding 416-series sockets or other hardware is a factor, as well as the simple and childish fact that you can see the glow of the 437A's heater.

The 416A led to several series of ceramic-metal triodes, all having a planar structure rather than the conventional glass-tube coaxial design. A planar triode is a "sandwich" of parts,

brazed together in a vacuum chamber using special tooling. For example, General Electric developed the 7077 in 1951 for low-noise RF amplifiers. In spite of the "obsolescence" of vacuum tubes, the 7077 and its descendants are still manufactured in Owensboro, Ky., by MPD, the firm that took over GE's tube manufacturing.

These planar triodes are made almost exclusively for the front ends of military pulsed radars, due to the high cost of manufacturing a receiving tube in the US, especially an exotic one. Few audiophiles have ever seen a 7077, and I enjoy their expressions when they are handed one. It is the size of an aspirin tablet, and is made of white ceramic and gold-plated metal contacts. Some people have called it a "funny looking transistor."

I can guarantee that you will never see 7077s or their many derivatives in audio equipment, due to wholesale prices in the US \$600-1000 region. As I said, most manufacturers of high-end audio equipment usually are only interested in reducing manufacturing costs, not producing amplifiers that sound or perform better.

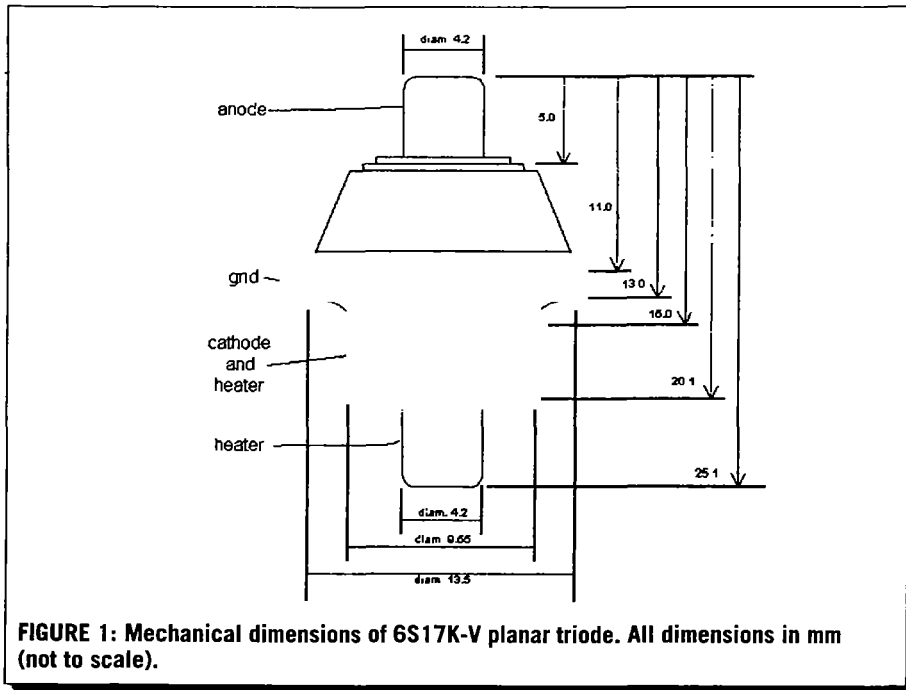


FIGURE 1: Mechanical dimensions of 6S17K-V planar triode. All dimensions in mm (not to scale).

AVAILABILITY


The high cost of such planars need not be an impediment to the home constructor. Many tube factories made their own planars over the years. A series of unique planar triodes was made at the Novosibirsk factory in Russia—these are similar internally to the American 7077 family, yet quite different in outward appearance. I have recently discovered that surplus Russian planars are available at very reasonable prices.

The easiest one to obtain is the 6S17K-V (usually called 6C17bB by Russian dealers). This device resembles a rocket nose-cone (Photo 1), not a vacuum tube. Intended for microwave frequencies, it has no base or contact pins—electrical contacts are smooth surfaces to minimize path lengths, thus reducing parasitic inductances and transmission-line effects (Fig. 1).

I have learned that surplus Russian tube dealers usually have a supply of 6S17K-Vs for sale for about \$30 apiece. These tubes are apparently no longer manufactured, yet I understand there are tens of thousands


It is not enough to put oil into a Capacitor to make it musical....

KRISTALL CAP

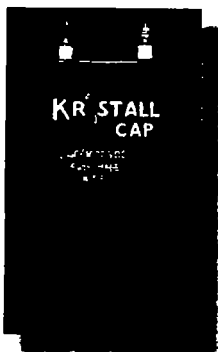

Forget about resistive devices for the volume setting. We offer a silver wired transformer approach

Silver Rock Transformer-Potentiometer

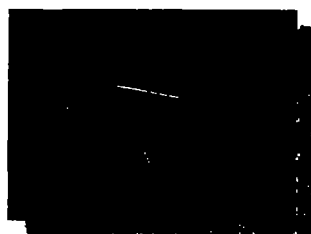

It is not enough to use silver wire for a good SE-OPT...

Silver Rock Output transformer



There is only one optimum solution for a given problem.

Audio Consulting / 14B chemin des Vignes / 1291 Commugny / Switzerland
 Fax: 00-41-22-960-12-59 / e-mail: serge.schmidlin@span.ch
<http://www.audio-consulting.ch>

sion and other grid effects, sometimes collectively called "contact potential." Thus, no biasing network or negative bias voltage was needed.

The EQ circuit is a classic which has been used many times. My previous experience with it was in my nu-

vistor phono preamp (*Glass Audio* 4/93, p. 6). Because of the very high voltage gain of the 6S17K-V, you can dispense with one whole gain stage. The output subminiature-tube stage provides moderate gain and a reasonably low output impedance.

CONSTRUCTION

Each channel was constructed on a custom IAG terminal board. The special mounting requirements of the 6S17K-V required some ingenuity.

I drilled holes in the IAG boards next to the location of the tube, as it is laid down on the board. A #4 screw and nut at each location holds a small contact finger cut from brass shim stock. The contact is bent to firmly contact the appropriate ring on the tube. If this is done properly, all the contacts will be solid, and the tube will be very firmly held in place. The submin tubes had long wire leads, which were wrapped around convenient turret terminals.

I mounted the two channel boards in

[See our new design](#)

IT'S HERE

[Read our latest product reviews](#)

[Visit our updated online catalog](#)

VISIT US TODAY

[Link to the websites you need](#)

[Find the clubs in your area](#)

COMPLETELY REENGINEERED

[Download software and product reviews](#)

[Shop Old Colony Sound Lab for books, test CDs, and more](#)

www.audioXpress.com

[Contact Us](#) and let us know what you think

6S17K-V CHARACTERISTICS

Heater: 6.3V 300mA
Anode voltage, maximum: 200V DC
Cathode current, maximum: 11mA
Anode dissipation, max: 2W
Grid dissipation, max: 0.1W
Transconductance: 14mA/V (14ms)
 μ , approximate: 80-185
Noise figure at 3GHz: 16.5dB
Microphony noise, max: 30mV (with anode load 2k Ω)
Input capacitance: 3pF
Output capacitance: 0.015pF
Grid-anode capacitance: 1.5pF

SUPPLIERS

IAG
PO Box 10096
Killeen, TX 76547-0096 USA
Phone/Fax 254-699-8702
E-mail hiag@dashlink.com


the .com

Your online source for name brand audio tubes

- Over 1000 types available online
- Perfect Pair matched power tubes
- Capacitors and sockets

Order online at thetubestore.com

or call toll free 1-877-570-0979

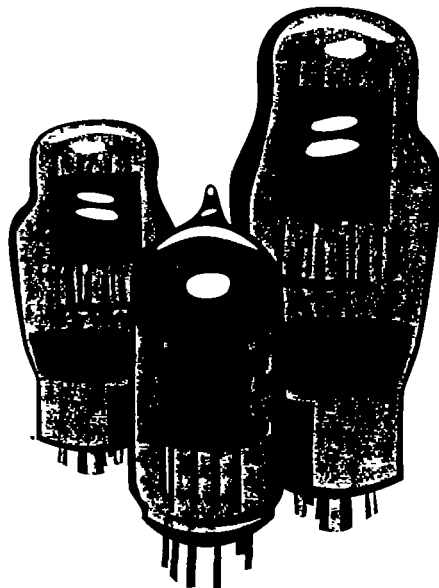

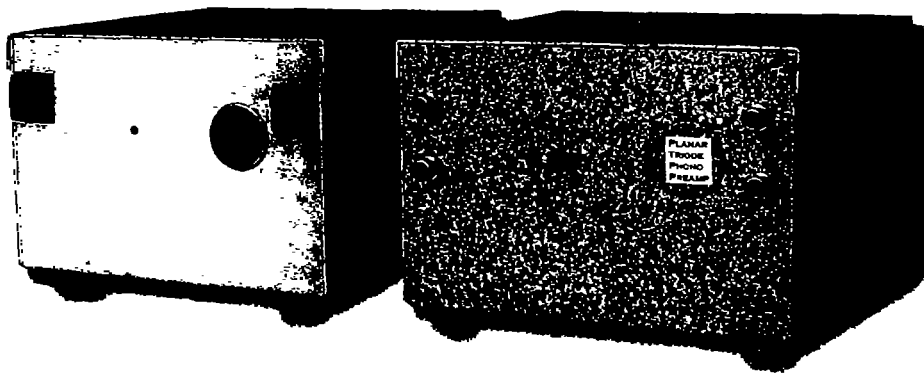


PHOTO 3: Left, power-supply chassis; right, preamp chassis.

a massive mild-steel box, which appears to be a surplus electrical enclosure (Photo 2). In spite of past claims that aluminum enclosures result in better sound, you need proper magnetic shielding here, so a steel cabinet is called for.

The power supply, which provides a great deal of filtering for low noise, is in a separate cabinet (Photo 3). This was a good place to apply one of the circuits developed for my switching-supply article (April 2001 *aX*), so I used Fig. 6, the supply based around a Maxim MAX1771 and a small transformer intended for making high voltage for electronic automotive ignition (Fig. 3). This supply easily makes about -100V at 15mA, plenty for this

circuit. By using heavy filtering and decoupling, the need for separate voltage sources for the two channels and for active regulation (often an additional source of noise) is eliminated.

I measured the B+ supply under load and found that with no signal into the preamp, noise and hum on the B- line was less than 5 μ V. A three-terminal regulator drops the +12V to approximately 6V for heater power. This IC is a 5V device—by using the old trick of forward-biased diodes between its return line and ground, the actual voltage is boosted to about 6.2V DC.

The +12V is obtainable from any suitable AC-DC plug-in power pack, or from a bench supply. This scheme even raises the possibility of a tube audio system powered from a 12V battery, making its use in an RV reasonable. (Provided the turntable is not used while the RV is in motion, of course.)

How does it sound? Very clean and transparent, much like my GA nuvistor preamp...and with a major improvement: the planar triodes are very non-microphonic, while nuvistors are notorious for having microphony problems. I mounted my previous nuvistor preamp's PC board on rubber shock mounts for a very good reason: high amplifier volumes easily gave a feedback howl. This circuit does not appear to need such mounting considerations.

I believe that this preamp gives some very costly and finicky commercial preamps a serious run for their money. Building this project will both save a large sum of money and permanently eliminate the audiophile's need to plug 6922s into a preamp and tap them each to find one that is less microphonic than the others. ♦

PARTS LIST


(R1–R10 and C1–C7 are for one channel; R11–R20 and C11–C17 for the other. All resistors 1/2W metal film unless noted; all capacitors 150V or greater metalized film unless noted.)

R1, R11	47k
R2, R12, R8, R18, R21–R25	470, 1W
R3, R13	51k, 1W
R4, R14	220k
R5, R15	10k
R6, R16	62k
R7, R17	1M Ω
R9, R19	180k
R10, R20	1k5
C1, C10, C6, C16	470n
C2, C12	10 μ F
C3, C13	33n
C4, C14	6.8n
C5, C15	1n
C7, C17	330 μ F 25V electrolytic
D1, D2	1N4001
Regulator	2A large TO220 package (NTE1934X or similar)
DC-DC converter	see text


Misc: (2) steel enclosures, AC adapter (Mouser 412-112153 or similar), SPST power switch rated 2 amps or more, (4) RCA panel-mount connectors, (2) IAG custom breadboards, wire.

VacuTrace™

Vacuum Tube Curve Tracer

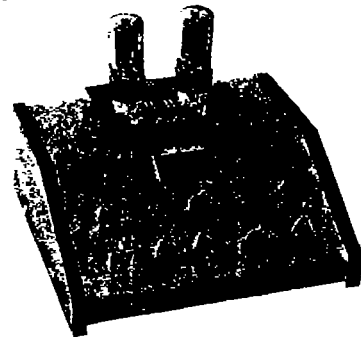

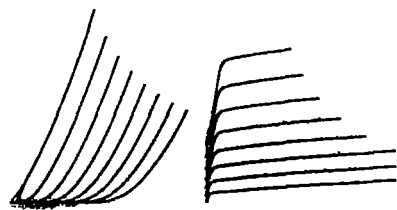See what you've been missing. Invest in a VacuTrace™ Assembled \$999. Kit \$899



www.hagtech.com

Hagerman Technology LLC
PO Box 26437
Honolulu, HI 96825 USA
Phone (808)-383-2704
Fax (808)-394-6076



HEAR FOR YOURSELF

The film capacitors chosen by many highly acclaimed manufacturers for use in their very best designs.

H O V L A N D

MusiCAP®

"If you want see-thru, high definition, detail and listenability, try the MusiCaps." Joe Roberts, **SOUND PRACTICES**, Issue 6

THE ULTIMATE CAP

The most naturally revealing capacitor. Film and foil polypropylene construction. Optimized for critical speakers and vacuum tube electronics. Silver-plated leads. Values from .01 to 10 μ F. Precision made in USA.

To experience MusiCaps for yourself, contact:

- Welbome Labs 303-470-6585
- Madsound Speaker Components 608-831-3433
- Antique Electronic Supply 480-820-5411
- Michael Percy Audio Products 415-669-7181
- The Parts Connection 800-769-0747
- Anchor Cross Co., Tokyo Japan 81-3-3203-5606
- Trevor Lees Audio, Australia 61-3-9853-2315
- Wilmslow Audio, England 44-01455-286603
- Tang Hill International Ltd Taiwan 8862-2-5813605
- Hong Kong Bush, Hong Kong 852-2525-3227
- Audio Parts, Korea 82-2-3272-2704
- Well Audio Lab, Singapore 65-3380368
- Knopf Hi-Fi, Germany 49-0211-33-17-76
- OEMs contact Hovland Company at ph 209-966-4377 • fax 209-966-4632

www.hovlandcompany.com